CHECKLIST

Reading a circuit diagram checklist

- [ ] Locate the power source and ground symbols
- [ ] Check for dots at line junctions to confirm connections
- [ ] Identify passive components like resistors and capacitors
- [ ] Spot active components such as transistors and diodes
- [ ] Note reference designators and match them to the parts list
- [ ] Verify polarity on batteries, capacitors and diodes
- [ ] Follow any switches or connectors to external points